## **Table of Contents**

Prelab 3	. 1
Part 1	. 1
Part 2	2

## Prelab 3

```
% Name: Logan Calder
% Lab Number: 2
% Class: ECEN 50L
% Date: 4/23/24
% Section time: 14:15T
```

## Part 1

```
Vs = 5;
Rs = 10e4;
Rvm = 10e5;
R1 = [15e3;20e3;30e3;56e3;100e3];
% Expected Value of v1
I = Vs./(Rs+R1);
V1 = Is .* R1;
% Expected value of v1L
R1vm = (R1.*Rvm)./(Rvm+R1);
Rt = (R1vm + Rs);
I = Vs./Rt;
V1L = I .* R1;
% Expected value of E1
E1 = (V1L - V1)./V1*100; % This is a provided formula
% Expected value of Rvm for known v1L
RmvL = V1L.*R1.*Rs./(Vs*R1-v1L.*(R1+Rs));
table_A = table (R1,V1,V1L, E1, RmvL)
table_A =
```

5×5 table

R1	V1	V1L	E1	RmvL
15000	0.65217	0.65343	0.19313	1.015e+06
20000	0.83333	0.83607	0.32787	1.02e+06
30000	1.1538	1.1617	0.67669	1.03e+06
56000	1.7949	1.8297	1.9406	1.056e+06

1e+05 2.5 2.619 4.7619 1.1e+06

## Part 2

```
Vs = 2;
Rs = 100;
Ram = 1e3;
R2 = [51,62,100,270,330];
% Expected value of i2
I2 = Vs./(Rs + R2) * 10e2;
% Expected value of i2L
I2L = Vs./(Rs + R2 + Ram) * 10e2;
% Expected % error
E2 = (I2L - I2)./I2 * 100; % This is really big but seems right
% Expected RamL value
RamL = ((Vs ./I2L) * 10e2 - Rs - R2);
R2 = R2';
I2 = I2';
I2L = I2L';
E2 = E2';
RamL = RamL';
table_B = table (R2,I2,I2L,E2,RamL)
table_B =
  5×5 table
    R2
             I2
                      I2L
                                 E2
                                           RamL
           13.245
                               -86.881
     51
                     1.7376
                                           1000
     62
           12.346
                     1.7212
                               -86.059
                                           1000
    100
               10
                     1.6667
                               -83.333
                                           1000
    270
           5.4054
                     1.4599
                               -72.993
                                           1000
```

Published with MATLAB® R2024a

4.6512

1.3986

330

-69.93

1000